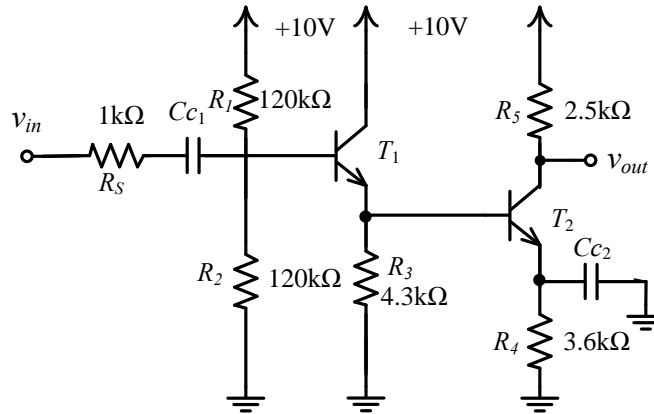


EHB222E Introduction to Electronics Homework 2

Deadline: 06/04/2015 (before the lecture)

1.




Two-stage BJT amplifier

Coupling capacitors C_{C1} and C_{C2} should take high values; you can select 1mF for both.

Transistor parameters : $\beta=300$, $V_{BE}=0.65V$, $V_T=25mV$, $V_A=100V$

- a. **Calculation:** Carry out a DC analysis for the circuit . Find DC operating values for I_{C1} , I_{C2} , V_{CE1} , and V_{CE2} .
- b. **Simulation:** Construct the above circuit using SPICE. Use the Fairchild 2N4124 model for the transistors. Find DC values of I_{B1} , I_{B2} , I_{C1} , I_{C2} , V_{in} , and V_{out} by performing bias point (DC operating point) analysis in SPICE. Compare the results with those calculated in part 1(a). Do they match well? Justify your answer.

2.

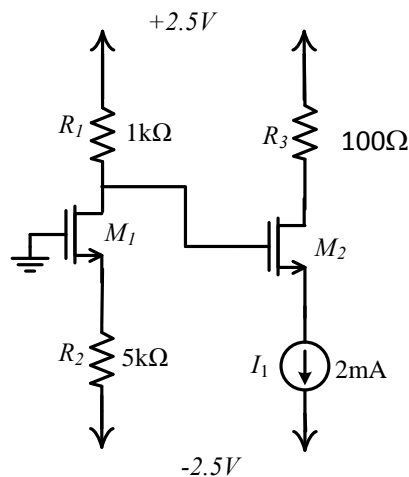

Transistor parameters : $V_T=0.76V$, $k_n'=126\mu A/V^2$, $\lambda=0$ ($V_A=\infty$), $(W/L)_1=(W/L)_2=13\mu/2\mu$

- a. Calculation:** Carry out a DC analysis for the circuit . Find DC operating values for I_{D1} , I_{D2} , V_{DS1} , and V_{DS2} .
- b. Simulation:** Construct the above circuit using SPICE. Use the T15DN model for the transistors; connect body terminals of the transistors to their source terminals. For details of using LTspice check out the tutorial attached to the homework. Find DC values of I_{D1} , I_{D2} , V_{DS1} , and V_{DS2} by performing bias point (DC operating point) analysis in SPICE. Compare the results with those calculated in part 2(a). Do they match well? Justify your answer.

Grading: 1(a)25 %, 1(b)25 %, 2(a)25 %, 2(b)25 %

*Note: Do not forget to attach SPICE **output file** prints to your homework!*


Mini LTspice Tutorial

Model parameters for NMOS and PMOS transistors are given below.


```
.MODEL T15DN NMOS (           LEVEL = 3
+TOX = 1.4E-8   NSUB = 1E17   GAMMA = 0.5483559
+PHI = 0.7     VTO = 0.7640855 DELTA = 3.0541177
+UO = 662.6984452 ETA = 3.162045E-6 THETA = 0.1013999
+KP = 1.259355E-4 VMAX = 1.442228E5 KAPPA = 0.3
+RSH = 7.513418E-3 NFS = 1E12   TPG = 1
+XJ = 3E-7     LD = 1E-13    WD = 2.334779E-7
+CGDO = 2.15E-10 CGSO = 2.15E-10 CGBO = 1E-10
+CJ = 4.258447E-4 PB = 0.9140376 MJ = 0.435903
+CJSW = 3.147465E-10 MJSW = 0.1977689 )
*
.MODEL T15DP PMOS (           LEVEL = 3
+TOX = 1.4E-8   NSUB = 1E17   GAMMA = 0.6243261
+PHI = 0.7     VTO = -0.9444911 DELTA = 0.1118368
+UO = 250     ETA = 0         THETA = 0.1633973
+KP = 3.924644E-5 VMAX = 1E6     KAPPA = 30.1015109
+RSH = 33.9672594 NFS = 1E12   TPG = -1
+XJ = 2E-7     LD = 5E-13    WD = 4.11531E-7
+CGDO = 2.34E-10 CGSO = 2.34E-10 CGBO = 1E-10
+CJ = 7.285722E-4 PB = 0.96443 MJ = 0.5
+CJSW = 2.955161E-10 MJSW = 0.3184873 )
```

In order to use the parameter sets, shown above, in Ltspice, please follow these steps:


- 1- Create a .txt file named T15D_models.txt.
- 2- Copy parameters above and paste them into T15D_models.txt file.
- 3- Then place T15D_models.txt file into the LTspice folder (or the folder where your project saved).
- 4- After click on the .op tab as shown in figure below (circled red), write ‘.include T15D_models.txt’ into the opened window. After pressing OK, you will see a rectangle information bar. Paste it somewhere in the schematic.

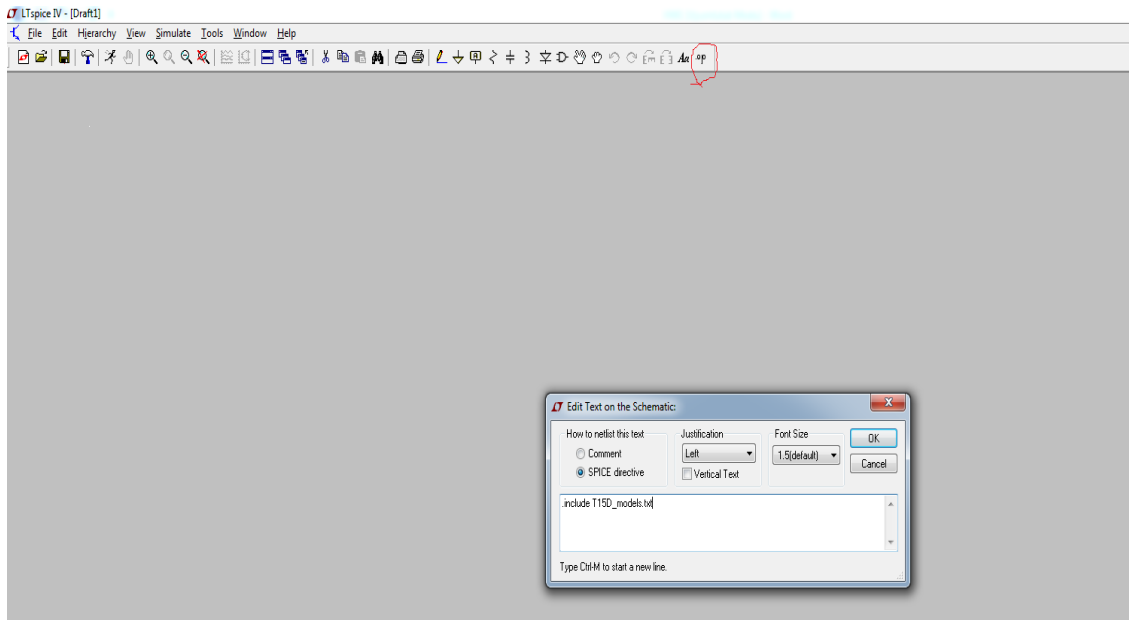

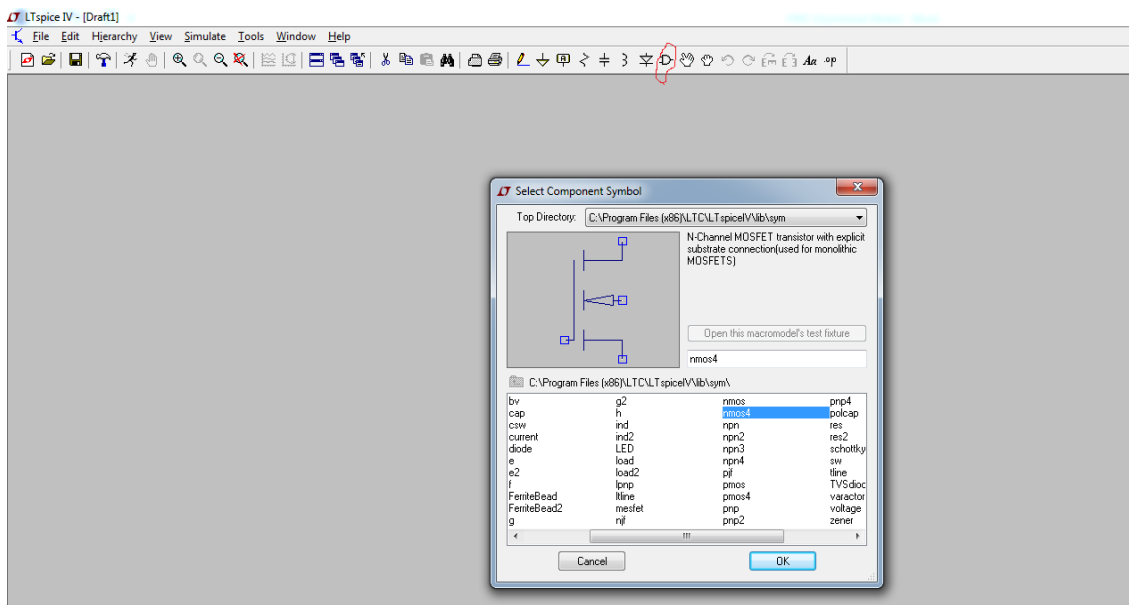
- 5- To add MOS transistors, click on the component tab shown below (circled red), then select NMOS4 and PMOS4.



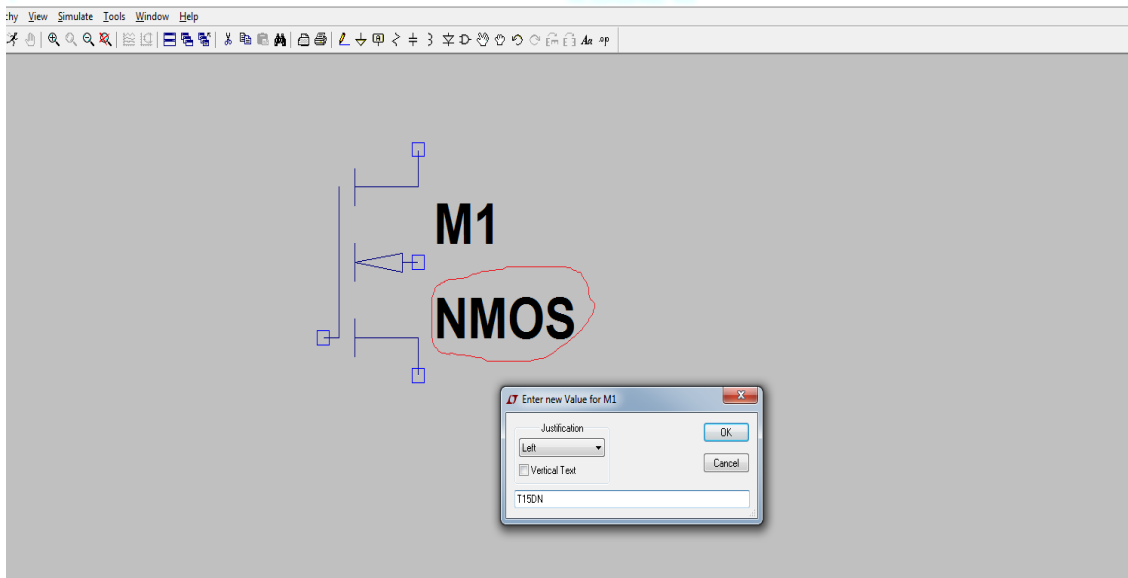- 6- After selecting the transistor, right click on the transistor; name it as T15DN for NMOS and T15DP for PMOS



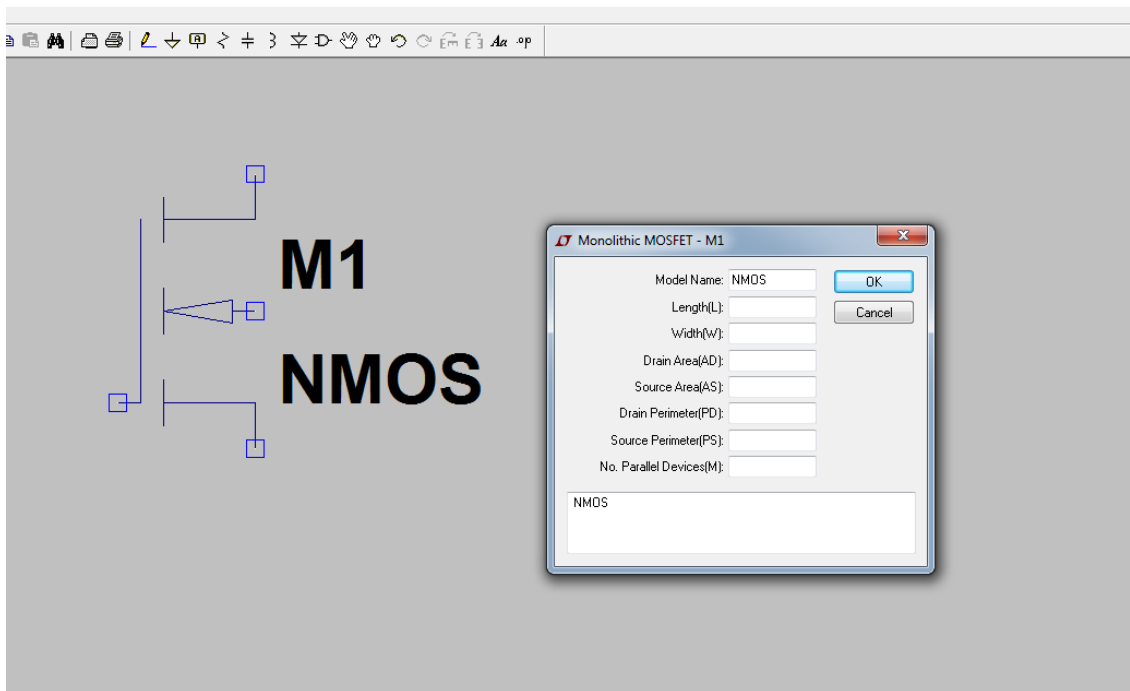7- To enter W and L parameter values, right click on the transistor and write W and L values.



Note: Your simulation results can be slightly different from hand calculations because of the probable mismatches between calculation and simulation parameters.