

Student Name:

Solutions

Instructor: Mustafa Altun

Student ID:

Date: 25/11/2016

BLG231E Digital Circuits Quiz 2

Duration: 20 Minutes


Grading: 1a) 50%, 1b) 50%

Quiz is in closed-notes and closed-books format

For your answers please use the space provided in the exam sheet

GOOD LUCK!

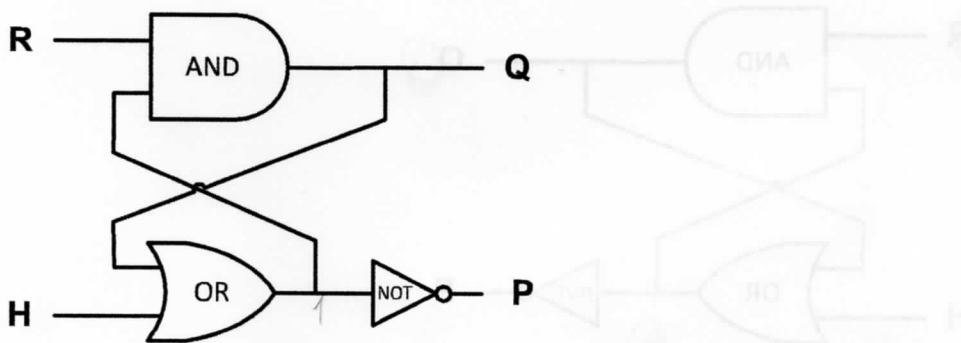1. Consider a sequential circuit shown below.



a) An expected operation of the circuit is having complemented logic values for **Q** and **P** outputs. Determine the restrictions on **R** and **H** so that **P** equals to **Q**. Fill in the truth table below with indicating the **bad conditions** or restricted cases

R	H	Q-pre	Q	P
0	0	0	0	1
0	0	1	0	1
0	1	0	0	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

} same \Rightarrow restricted

b) Suppose that the inverter has a delay of **1ns**; the AND gates has a delay of **2ns**; and the OR gate has a delay of **5ns**. Sketch the **waveforms at the outputs Q and P** if the input signals R and H shown below are applied. Suppose that initial values of Q and P are logic 0 and 1, respectively.

