

EHB262E Electronics II, Fall 2012 FINAL

Duration: 120 Minutes

Grading: 1) 30% (6% each), 2) %30, 3) 40% (25%+15%)

Exam is in closed-notes and closed-books format


For your answers please use the space provided in the exam sheet

GOOD LUCK!

1) Please circle TRUE if you think that the statement is true; FALSE otherwise.


- a. The characteristic curve of an **analog** amplifier is shown below. The region circled by the dashed line is where the amplifier operates properly.

TRUE / FALSE

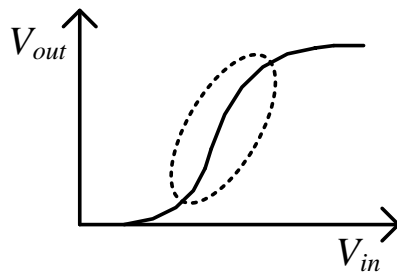


- b. For the circuit shown below, $v_{out} = -RC \frac{dv_{in}}{dt}$.

TRUE / FALSE

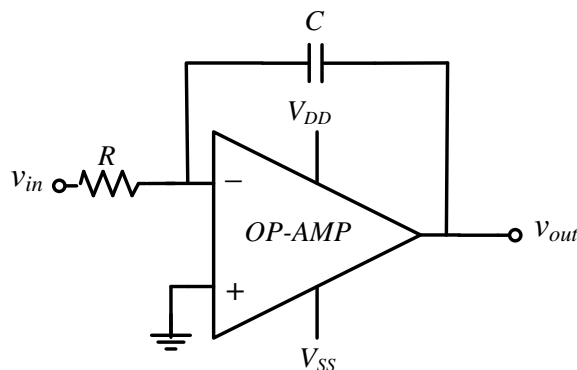


- c. For the amplifier shown below, $\frac{v_{out}}{v_{in1} + v_{in2}} = -\frac{r_{o1} // r_{o2}}{g_{m1} \cdot g_{m2}}$ (Suppose that the transistors are in **saturation**).

TRUE / FALSE

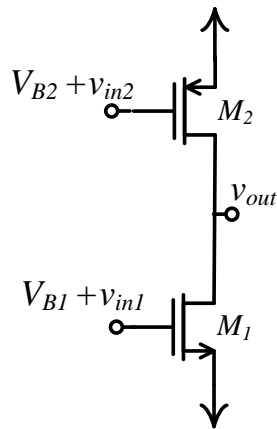


- d. Consider a circuit shown below where $I_{D1} = 1\text{mA}$ and $R_1 = 2\text{k}\Omega$. Suppose that M_1 and M_2 are identical transistors. If R_2 is $3\text{k}\Omega$ then M_2 operates in **triode** (linear) region.

TRUE / FALSE

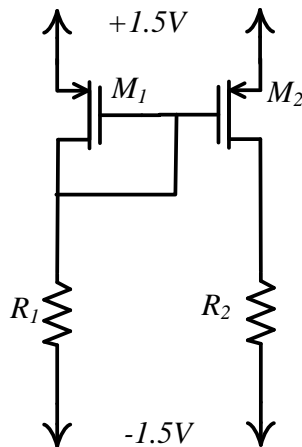

- e. For the Darlington pair shown below, $\frac{I_C}{I_B} = \beta_1 + \beta_2$.


TRUE / FALSE

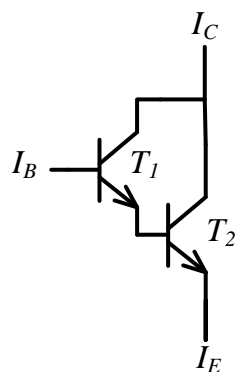

- 2) Consider a two-stage amplifier shown below where $V_B = -0.4V$. Suppose that the value of C_c is high enough, so it can be considered shorted in small signal analysis. Find the small signal values of r_{in} , r_{out} , and v_{out}/v_{in} .

NPN Transistor parameters: $V_{BE} = 0.7, \beta = 100, V_A = 100V, V_T = 25 mV$.

PNP Transistor parameters: $|V_{BE}| = 0.7, \beta = 50, |V_A| = 10V, V_T = 25 mV$.

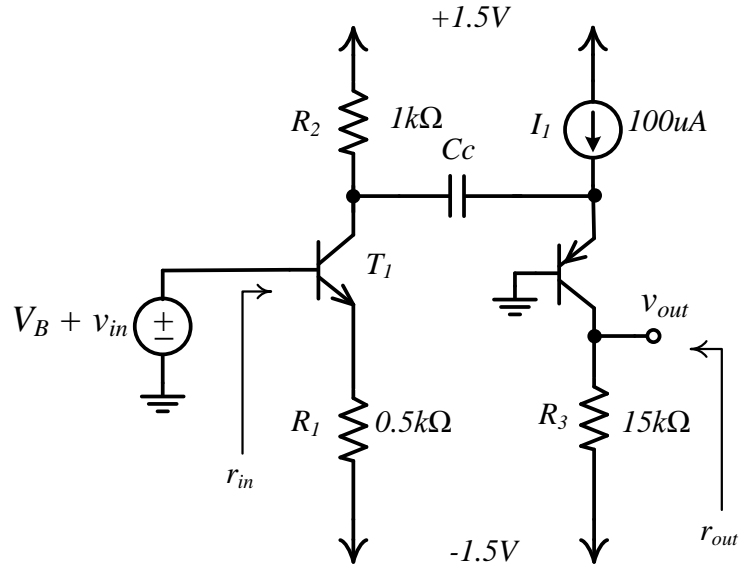


Two-stage Amplifier.

- 3) Consider an operational amplifier shown below. Suppose that input and output DC values are all zero. In DC analysis, use the following equation:

$$I_D = \frac{1}{2} k'_{p,n} \frac{W}{L} (V_{GS} - V_{T0,p,n})^2.$$


Transistor parameters: $k_n' = \mu_n c_{ox} = 100 \mu\text{A}/\text{V}^2$, $k_p' = \mu_p c_{ox} = 50 \mu\text{A}/\text{V}^2$, $V_{An} = 25\text{V}$, $|V_{Ap}| = 25\text{V}$, $V_{T0,n} = 1\text{V}$, $|V_{T0,p}| = 0.5\text{V}$.

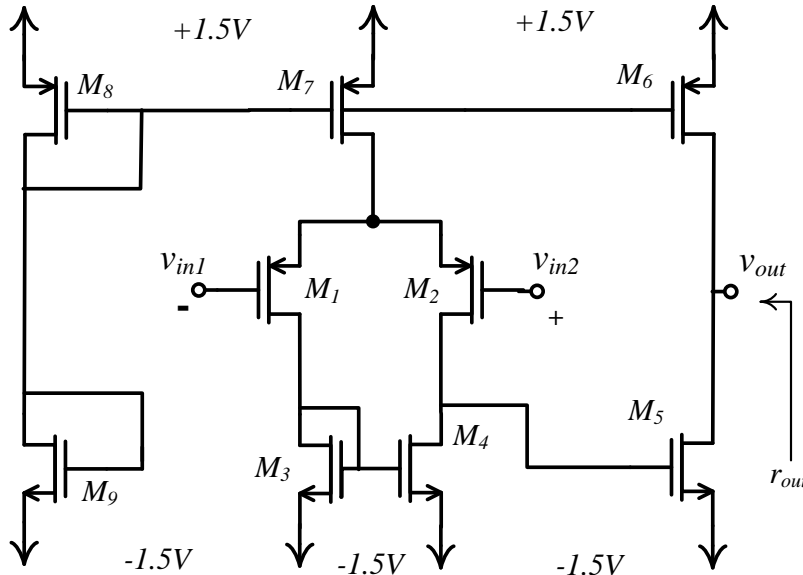

Transistor	L (μm)	W (μm)
M_1	1	32
M_2	1	32
M_3	1	16
M_4	1	16
M_5	1	16
M_6	1	8
M_7	1	16
M_8	1	16
M_9	1	2

Operational Amplifier (OP-AMP).

- Find the small signal values of the differential gain $v_{out} / (v_{in2} - v_{in1})$, the common-mode gain v_{out} / v_{in} (where $v_{in} = v_{in2} = v_{in1}$), and the output resistance r_{out} of the amplifier. Also determine the **CMRR**.
- Consider a non-inverting amplifier shown below where $R_1 = R_2 = 50\Omega$. If you use an **ideal** OP-AMP then what is v_{out} / v_{in} ? If you use the OP-AMP shown above (use the results in **a.**) then what is v_{out} / v_{in} ? Justify your answer.

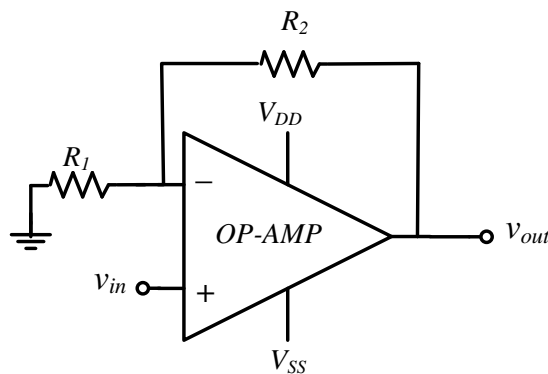

Non-inverting Amplifier

