

— Home Work - 1

1)  $n \cdot p = n_i^2$  ,  $n = p = 4 \cdot 10^{10}$  for intrinsic silicon ①

After doping Boron;

$$p_p \approx N_A = 10^{14}$$

$$n_p = \frac{n_i^2}{N_A} = \frac{16 \cdot 10^{20}}{10^{14}} = 1.6 \cdot 10^{10}$$

2)  $\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = V_T$

$$\Rightarrow \mu_p = \frac{D_p}{V_T} = \frac{16 \text{ cm}^2/\text{s}}{0.025 \text{ V}} = 640 \text{ cm}^2/\text{Vs}$$

$$\mu_n = \frac{D_n}{V_T} = 1440 \text{ cm}^2/\text{Vs}$$

P type ;  $N_A \gg n_p \Rightarrow p_p = \frac{1}{q(N_A \cdot \mu_p)} = 1.4 \cdot 10^{16} / \text{cm}^3$   
↳ e density in p type

N type ;  $N_D \gg p_n \Rightarrow n_n = \frac{1}{q N_D \mu_n} = 1.2 \cdot 10^{16} / \text{cm}^3$   
↳ hole density in n type

Remark;  $N_A > N_D$  ,  $\mu_n > \mu_p$  (in a pn-junction)

$$\Rightarrow V_0 = V_T \ln \left( \frac{N_A \cdot N_D}{n_i^2} \right) = 0.025 \text{ V} \cdot \ln \left( \frac{1.4 \cdot 1.2 \cdot 10^{32}}{10^{20}} \right) = 0.704 \text{ V}$$

$$W = x_n + x_p \text{ depletion width.} \quad (2)$$

$$W = \sqrt{\frac{2 \cdot \epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right) (V_0 + V_e)} \quad \left. \vphantom{W} \right\} \text{zero bias} \Rightarrow V_L = 0$$

$$W = \sqrt{\frac{2 \cdot 12 \cdot 8,85 \cdot 10^{-12}}{1,6 \cdot 10^{-19}} \left( \frac{1}{1,2 \cdot 10^{16}} + \frac{1}{1,4 \cdot 10^{16}} \right) \cdot 0,7V}$$

$$= \sqrt{\frac{2 \times 12 \times 8,85 \cdot 10^{-10} \text{ F/cm}}{1,6 \cdot 10^{-19}} \left( \frac{2,64 \cdot 10^{-16}}{1,4 \times 1,2 \cdot 10^{16}} \right) \text{ cm}^3 \cdot 0,7V} = 3,8 \mu\text{m}$$

$$c) \quad z_p = \frac{L_p^2}{D_p}, \quad z_n = \frac{L_n^2}{D_n}$$

$$L_p = \sqrt{D_p z_p} = \sqrt{16 \text{ cm}^2/\text{s} \cdot 0,2 \cdot 10^{-6} \text{ s}} = 3,6 \mu\text{m}$$

$$L_n = \sqrt{z_n D_n} = \sqrt{36 \text{ cm}^2/\text{s} \cdot 0,2 \cdot 10^{-6} \text{ s}} = 5,4 \mu\text{m}$$

$$I = A q n_i^2 \left( e^{V/V_T} - 1 \right) \left( \frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$$

$$= 0,001 \text{ cm}^2 \cdot 1,6 \cdot 10^{-19} \cdot 10^{20} / \text{cm}^3 \left( e^{0,7/0,025} - 1 \right) \left( \frac{16 \text{ cm}^2/\text{s}}{3,6 \cdot 10^{-4} \text{ cm} \cdot 1,2 \cdot 10^{16} / \text{cm}^3} + \frac{36 \text{ cm}^2/\text{s}}{5,4 \cdot 10^{-4} \text{ cm} \cdot 1,4 \cdot 10^{16} / \text{cm}^3} \right)$$

$$= 0,2 \text{ A}$$

$$\frac{I_{D1} = I_S (e^{V_1/nVT} - 1)}{I_{D2} = I_S (e^{V_2/nVT} - 1)} \Rightarrow \frac{I_{D1}}{I_{D2}} \approx \frac{I_S}{I_S} \frac{e^{V_1/nVT}}{e^{V_2/nVT}} \quad (2)$$

$$\frac{I_{D1}}{I_{D2}} = e^{(V_1 - V_2)/nVT}$$


$$\frac{7.2 \text{ mA}}{1.36 \text{ mA}} = e^{(0.05)/0.075 \cdot n}$$

$$n = \frac{0.05}{0.075 \cdot \ln\left(\frac{I_{D1}}{I_{D2}}\right)} = 1.2$$

$$\Rightarrow 7.2 \text{ mA} = I_S \cdot e^{0.05/1.2 \cdot 0.075} \Rightarrow I_S \approx 10^{-13} \text{ A}$$



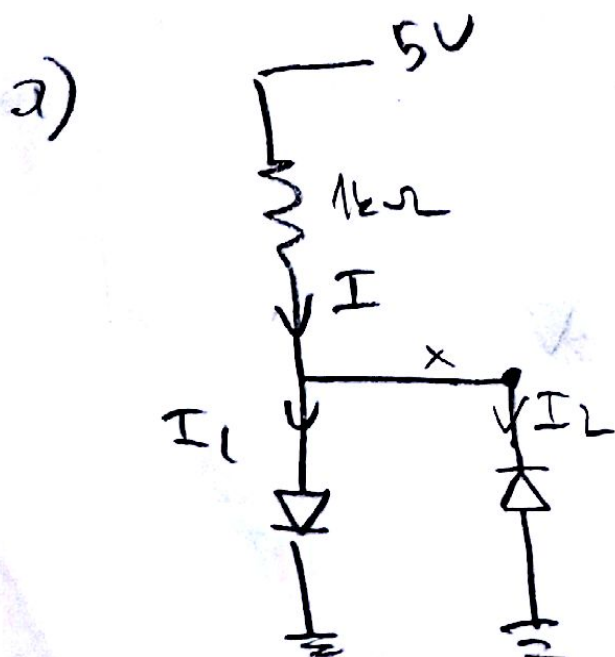$\Rightarrow$   $i-v$  characteristic of ideal diode.




$$V_x > 0 \Rightarrow I_2 = 0$$

$$V_x = V_D = 0.7 \text{ V}$$

$$5 - I_1 \cdot 1 \text{ k}\Omega - 0.7 \text{ V} = 0$$


$$I_1 = 4.3 \text{ mA}$$

4

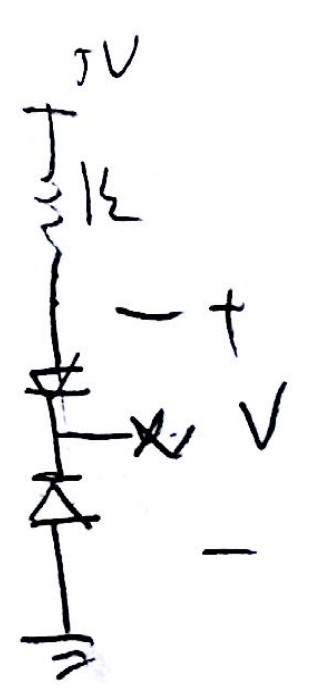

$$V_x \geq 0 \Rightarrow I = 0$$

$$V = 5V$$

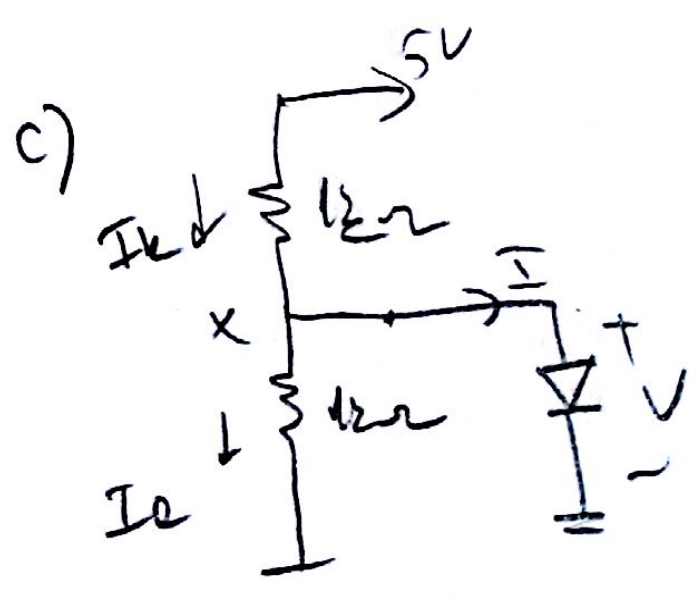


$$V_{\text{min}} = 0,7V$$

$$\frac{5 - 0,7}{1k} = I_k = 4,3mA$$

$$I_k = I_2 + I = \frac{0,7V}{1k} + I = 4,3mA$$

$$I = 3,6mA$$

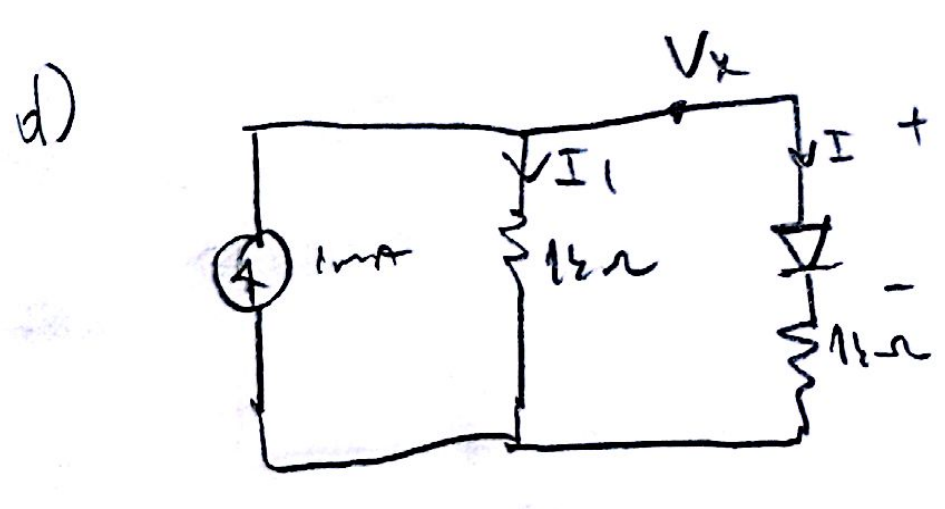

Assuming diode conducts

$$1mA = I_1 + I$$

$$V_x = I_1 \cdot 1k\Omega = 0,7V + 1k\Omega I$$

$$(I_1 - I) 1k\Omega = 0,7V$$

$$I_1 - I = 0,7mA$$


$$I_1 + I = 1mA$$

$$I_1 = 0,85mA$$

$$I = 0,15mA$$

$$V = 0,7V$$



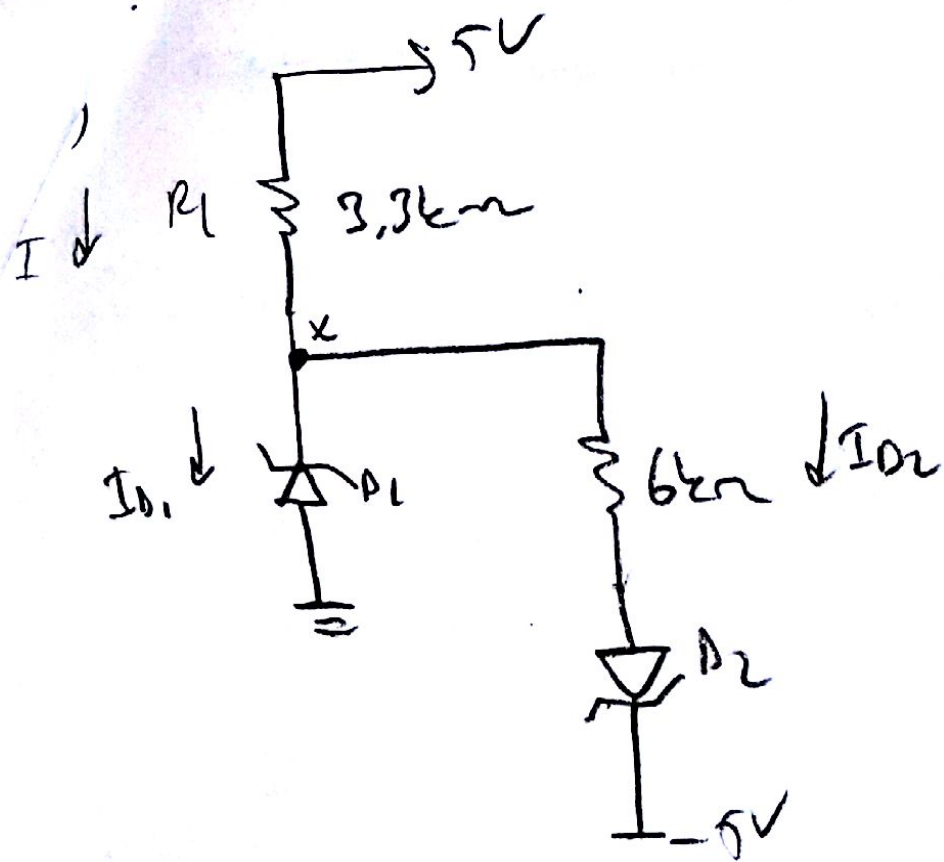

If  $D_2$  conducts, then  $V_x \geq 3$  (5)

Assuming  $V_x = 3V$

$$\Rightarrow \frac{3 - 0.7V + 5V}{6k\Omega} = I_{D2}$$

$$\frac{7.3V}{6k\Omega} = I_{D2} = 1.22 \text{ mA}$$


$$I = \frac{2}{3.3k\Omega} = 0.6 \text{ mA}$$

But  $I$  must be bigger than  $I_{D2}$   
 therefore  $I_{D1}$  must be equal to zero.

Assuming only  $I_{D2}$  conducts;

$$I_{D2} = I = \frac{5 - 0.7}{3.3k\Omega} = 1 \text{ mA} \Rightarrow 5 - 3.3V = 1.7V = V_x = 1.7V$$

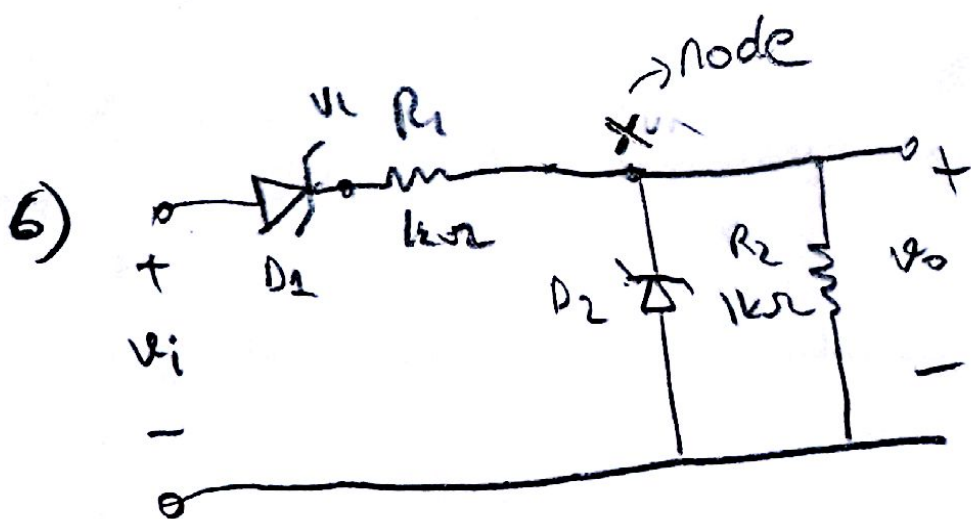Since  $V_x = 1.7V < 3V \Rightarrow I_{D1} = 0$



$V_x$ : voltage of node x

i) Positive alternant;

Case-1

$$0.7 > v_i > 0 \Rightarrow I_{D1} = 0, V_1 = 0, V_o = 0$$

Case 2

$$4.7 > v_i > 0.7 \Rightarrow D_1 \text{ conducts}$$

$$V_{1 \text{ max}} = 4.3V$$

$$V_{o \text{ max}} = V_{R2} = 2V$$

$$I_{D1} = 2 \text{ mA}$$

Case-3

$$v_i > 4.7V \Rightarrow I_{D1 \text{ max}} = 2.3 \text{ mA}$$

1) Negative alternans;

case 1;

$-2,7V < V_i < -0,7V \Rightarrow I_{D2} = 0, V_o = 0$  up to  $V_i = -2,7V$

case 2;

$V_i < -2,7V \Rightarrow$

$V_{o\min} = -0,7V$

$V_{x\min} = -4,3V$

$D_1$  conducts

$I_{D1\max} = I_{R1\max} = \frac{4,3 - 2}{1k} = 2,3mA$

$I_{D2\max} = 2,3mA - 0,8mA = 1,6mA$

