
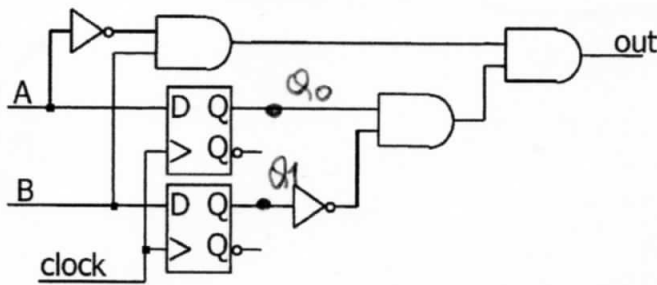


BLG231E Digital Circuits Homework 3

Deadline: 30/12/2016 (before 9:30)

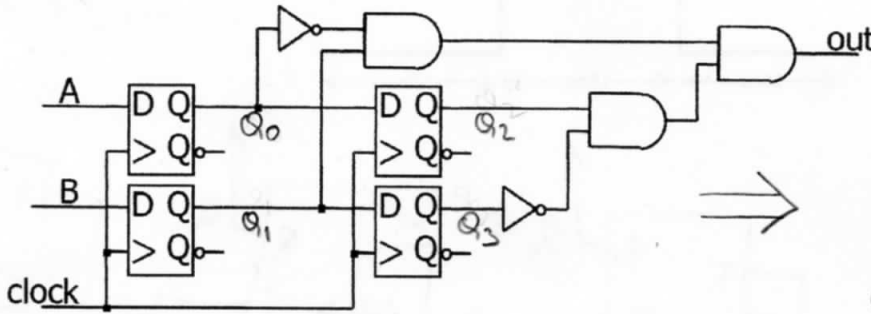1. SEQUENTIAL CIRCUITS: CIRCUITS TO STATES

Consider sequential circuits shown below.




1) a) State Table of 1st-Circuit

| AB | Q_0 | Q_1 | Q_2 | Q_3 | Q_0 | Q_1 | Q_2 | Q_3 |
|----|-------|-------|-------|-------|-------|-------|-------|-------|
| 00 | 0 | 0 | X | X | 0 | 0 | 0 | 0 |
| 00 | 0 | 1 | X | X | 0 | 0 | 0 | 1 |
| 00 | 1 | 0 | X | X | 0 | 0 | 1 | 0 |
| 00 | 1 | 1 | X | X | 0 | 0 | 1 | 1 |
| 01 | 0 | 0 | X | X | 0 | 1 | 0 | 0 |
| 01 | 0 | 1 | X | X | 0 | 1 | 0 | 1 |
| 01 | 1 | 0 | X | X | 0 | 1 | 1 | 0 |
| 01 | 1 | 1 | X | X | 0 | 1 | 1 | 1 |
| 10 | 0 | 0 | X | X | 1 | 0 | 0 | 0 |
| 10 | 0 | 1 | X | X | 1 | 0 | 0 | 1 |
| 10 | 1 | 0 | X | X | 1 | 0 | 1 | 0 |
| 10 | 1 | 1 | X | X | 1 | 0 | 1 | 1 |
| 11 | 0 | 0 | X | X | 1 | 1 | 0 | 0 |
| 11 | 0 | 1 | X | X | 1 | 1 | 0 | 1 |
| 11 | 1 | 0 | X | X | 1 | 1 | 1 | 0 |
| 11 | 1 | 1 | X | X | 1 | 1 | 1 | 1 |

- Obtain **state diagrams** and **state tables** of these two circuits.
- Determine whether these circuits are **Mealy** or **Moore** machines.
- Find the input conditions these circuits aim to recognize.
- Explain the differences in terms of working principles of these two circuits.

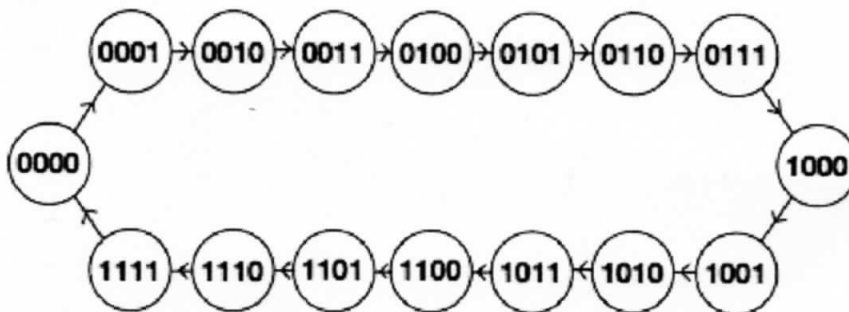2. SEQUENTIAL CIRCUITS: STATES TO CIRCUITS

Consider a state diagram shown below. Implement this state diagram using T (toggle) flip-flops and AND gates. What is the purpose of the circuit?



1-a) continues

State Table of 2nd Circuit

| AB | Q_0^c | Q_1^c | Q_0 | Q_1 |
|----|---------|---------|-------|-------|
| 00 | X | X | 0 | 0 |
| 01 | X | X | 0 | 1 |
| 10 | X | X | 1 | 0 |
| 11 | X | X | 1 | 1 |


Output Truth Table of 1st Circuit

| Q_0^c | Q_1^c | Q_2^c | Q_3^c | out |
|---------|---------|---------|---------|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |


Output T.T. of 2nd Circuit

| A | B | Q_0 | Q_1 | out |
|---|---|-------|-------|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

State Diagram of the 1st Circuit

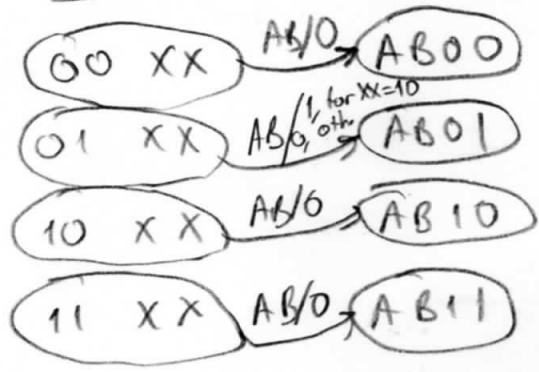

S.D. of the 2nd Circuit

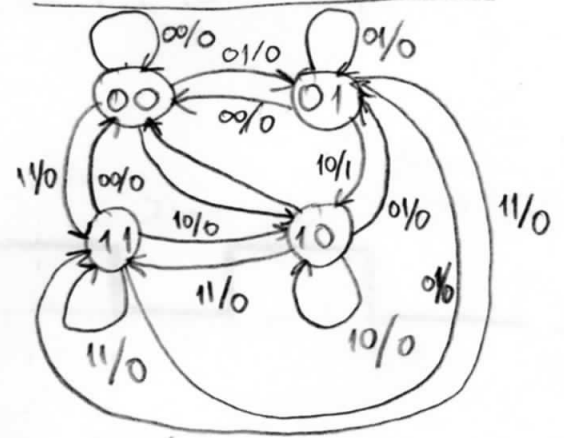


b) 1st Circuit \Rightarrow Moore machine, output depends only on current states
 2nd Circuit \Rightarrow Mealy machine, output depends on both current input and current states.

c) 1st Circuit \Rightarrow The circuit aims to recognize when previous input is 01 and current $Q_2 Q_3$ is 10
 2nd Circuit \Rightarrow Aiming to recognize when the current input is 01 and current $Q_0 Q_1$ is 10.

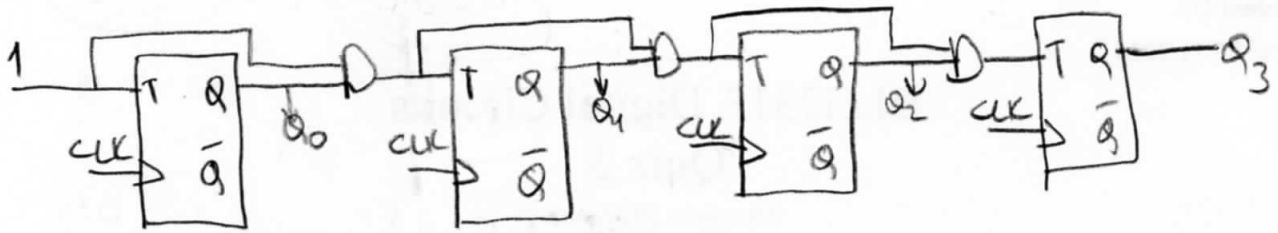d) In 1st circuit, the inputs only determines the next state, output is only determined by current states. However, 2nd circuit uses inputs for determination of both outputs and next states.

2-) It is an up counter circuit. Up counter with T-FFs and AND gates:



| Q_3^C | Q_2^C | Q_1^C | Q_0^C | Q_3 | Q_2 | Q_1 | Q_0 |
|---------|---------|---------|---------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |

5-


| | Grouped by | output | | | Re-Grouped By Next States | Re-Grouped By N. S. | | |
|---|------------|--------|-----|---|---------------------------|---------------------|-----|---|
| | | X=0 | X=1 | Z | | X=0 | X=1 | Z |
| ① | a | ① | ② | 1 | ① | ③ | ⑤ | 1 |
| | b | ② | ② | 1 | ② | ③ | ⑤ | 1 |
| | c | ② | ② | 1 | ③ | ⑤ | ⑤ | 1 |
| | e | ① | ② | 1 | ③ | ⑤ | ⑤ | 1 |
| | j | ① | ② | 1 | ③ | ⑤ | ⑤ | 1 |
| ② | d | ① | ① | 0 | ① | ① | ⑤ | 0 |
| | f | ① | ① | 0 | ① | ② | ③ | 0 |
| | h | ① | ① | 0 | ① | ② | ③ | 0 |
| | i | ① | ① | 0 | ① | ② | ③ | 0 |
| | | | | | | | | |

(This table does not need to be re-grouped)

So minimum 5 states is needed.

| | X=0 | X=1 | Z | |
|-------|-----|-----|---|---|
| ① → a | d | b | f | 1 |
| ② → e | b | f | f | 1 |
| ③ → b | d | a | e | 0 |
| ④ → d | e | e | f | 1 |
| ⑤ → f | f | a | b | 0 |

(Reduced state table)

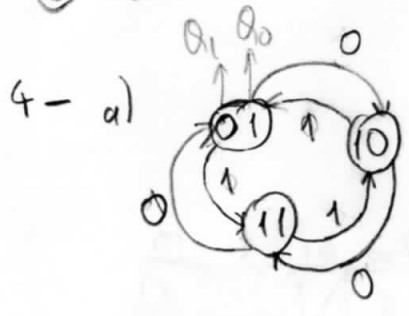

| Q_1^C | Q_0^C | I | Q_1 | Q_0 |
|---------|---------|---|-------|-------|
| 0 | 0 | 0 | X | X |
| 0 | 0 | 1 | X | X |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 |

| Q_0^C | Q_1^C | Q_0^C | I | Q_0 |
|---------|---------|---------|----|-------|
| 00 | 01 | 11 | 10 | |
| 0 | X | 0 | 1 | 1 |
| 1 | X | 1 | 0 | 1 |

$$Q_0 = \overline{Q_0^C} + \overline{I} \cdot Q_1^C + I \cdot Q_1^C$$

| Q_1^C | Q_0^C | I | Q_1 |
|---------|---------|----|-------|
| 00 | 01 | 11 | 10 |
| 0 | X | 1 | 0 |
| 1 | X | 1 | 1 |

$$Q_1 = \overline{Q_1^C} + I \cdot Q_0^C + \overline{I} \cdot \overline{Q_1^C}$$
