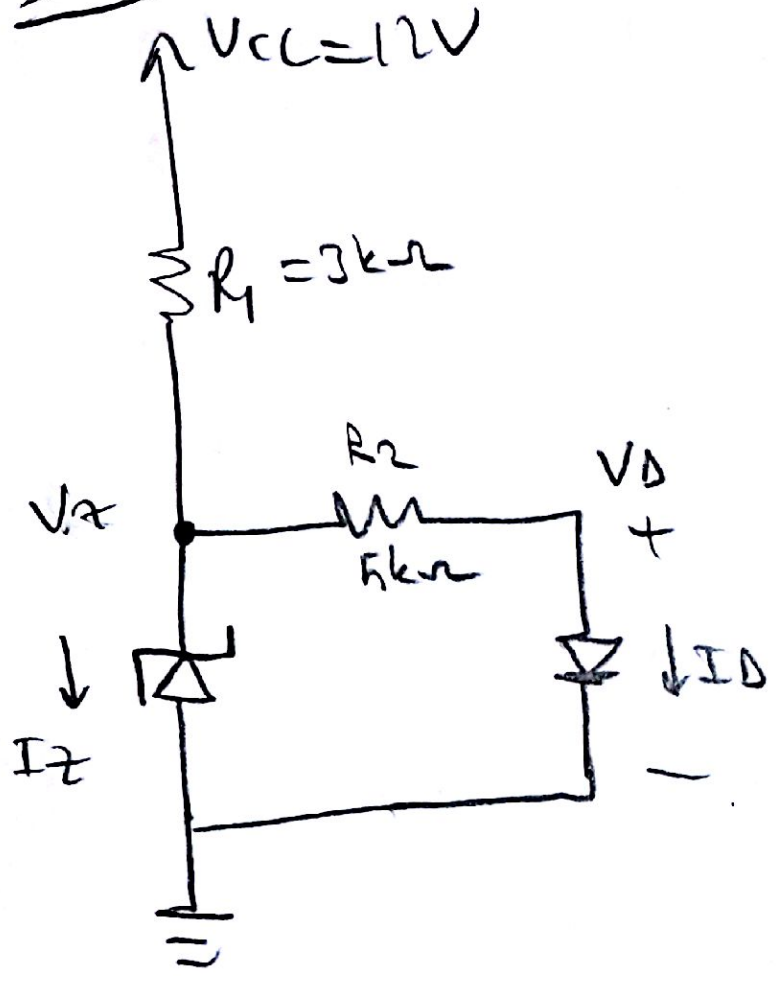


Uygulama



$V_T = 0,026 V$

$\Rightarrow V_{CC} = 12V, R_1 = 3k\Omega, R_2 = 5k\Omega$

$V_Z = 5,6V, I_S = 10^{-15} A$

find  $I_D, I_Z$  and  $V_D$

①  $I_D = \frac{V_Z - V_D}{R_2}$

②  $I_D = I_S (e^{V_D/V_T} - 1)$

But this is not a linear equation system

Therefore we must do iterations for solution.

from equation 1&2 we can write

$V_D = V_T \ln \left( \frac{V_Z - V_D}{R_2 \cdot I_S} + 1 \right)$  ③

First we choose a reasonable  $V_{D1}$  and we write it to eq. ③ and we get the second value for  $V_{D2}$ . Then we write  $V_{D2}$  into the right side of the eq. ③

$V_{D_{i+1}} = V_T \ln \left( \frac{V_Z - V_{Di}}{R_2 \cdot I_S} + 1 \right)$

$V_{D1} = 0,7 \rightarrow V_{D2} = 0,7178$

$V_{D2} = 0,7178 \rightarrow V_{D3} = 0,7177$

$V_{D3} = 0,717 \rightarrow V_D = 0,7177$

So we would have  $V_D = 0,7177$


And then

$$I_D = \frac{5,6 - 0,717}{5k\Omega} = 0,976 \text{ mA}$$

$$I_{R1} = \frac{V_{CC} - V_Z}{R_1} = \frac{12 - 5,6}{3k\Omega} = 2,13 \text{ mA}$$

$$\Rightarrow I_Z = I_{R1} - I_D = 1,15 \text{ mA}$$


Ungaben - 2

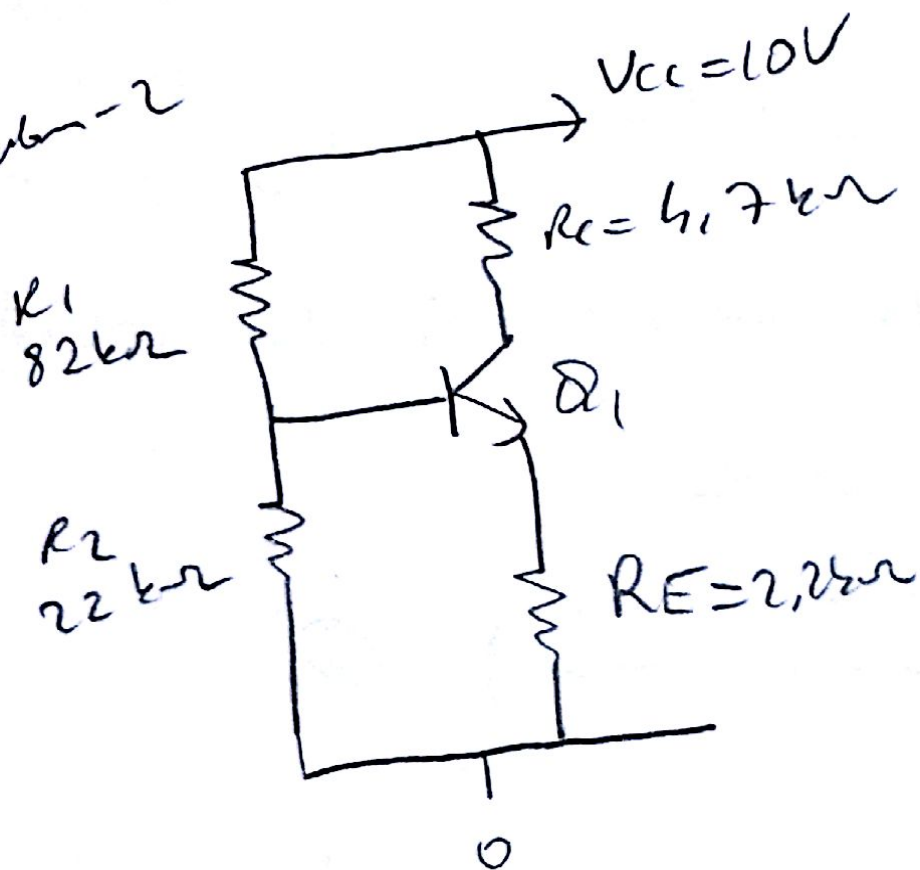

$\beta_F = 200$   
 $V_{BE} = 0,7V$   
 $I_C = ?$

Assuming  $Q_1$  is in forward active region  
 equivalent to; ( $I_{BQ1}$  is very small)

⇓ Circuit is

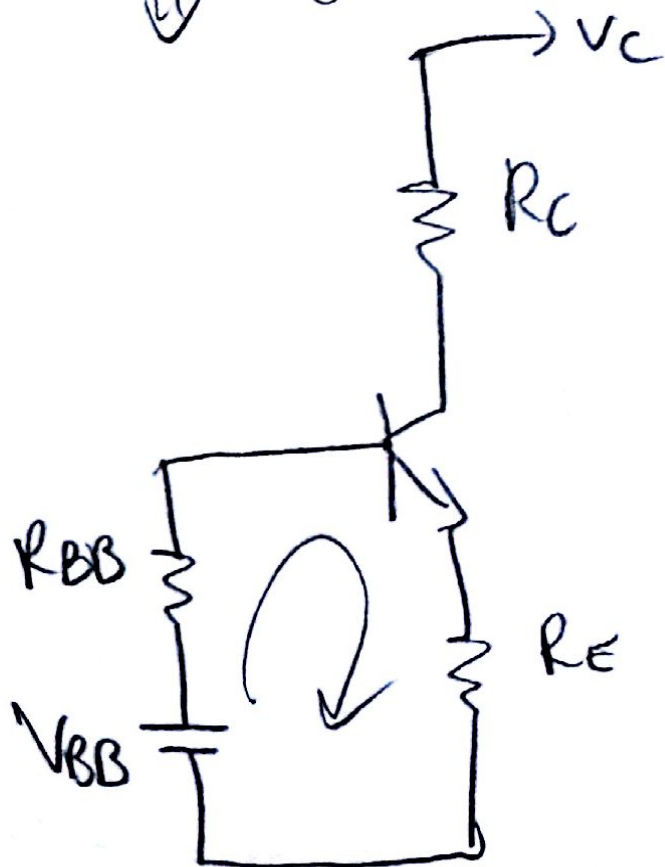


$$R_{BB} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2} = 17,34$$

$$V_{BB} = V_{CC} \cdot \frac{R_2}{R_2 + R_1} = 2,12V$$

$$\Rightarrow V_{BB} - \frac{I_C}{\beta_F} \cdot R_{BB} - 0,7V - I_C \left(1 + \frac{1}{\beta_F}\right) \cdot R_E = 0$$

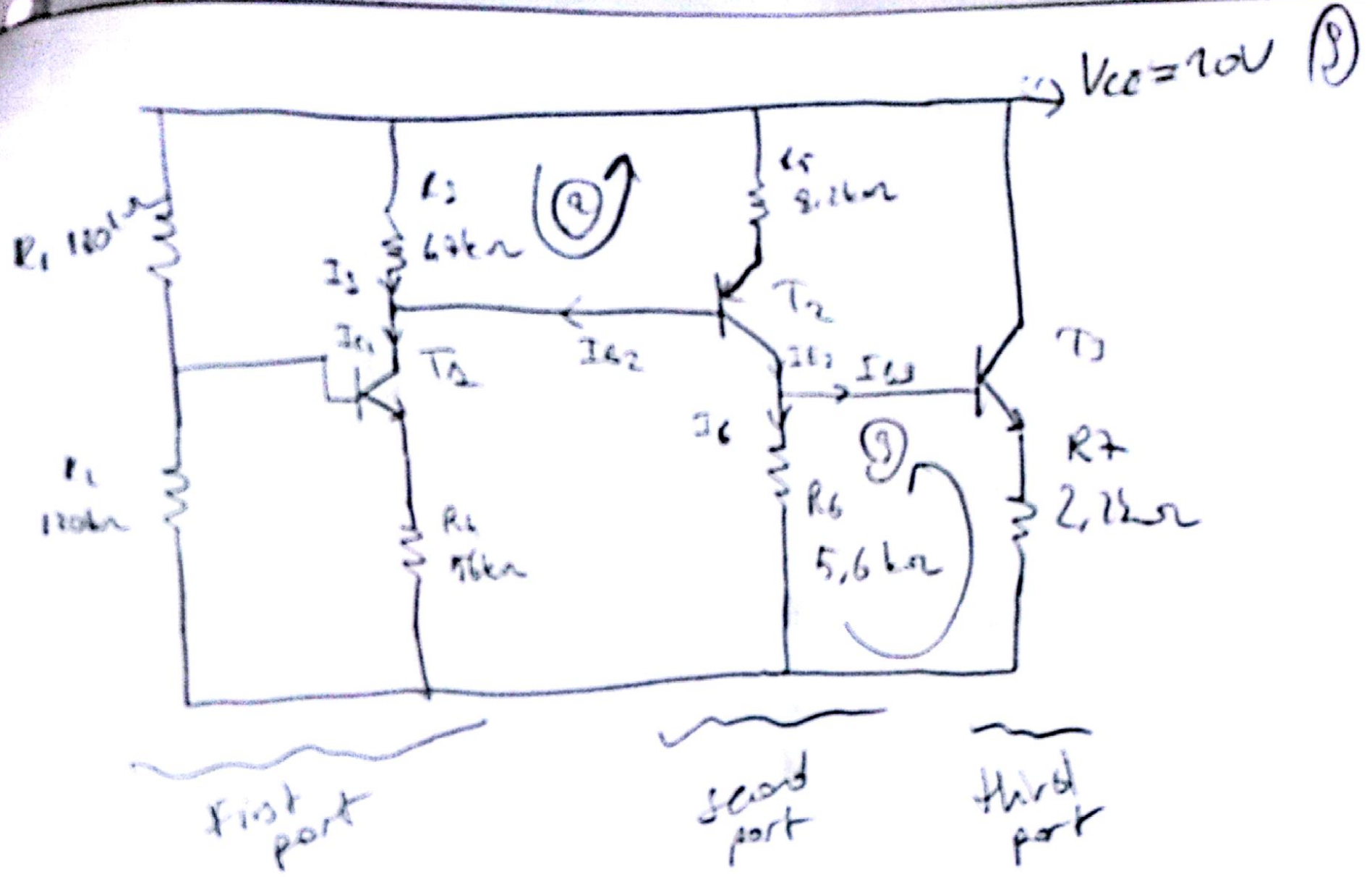
$$\Rightarrow I_C = \frac{V_{BB} - 0,7V}{\frac{R_{BB}}{\beta_F} + \left(1 + \frac{1}{\beta_F}\right) R_E} = 0,62 \text{ mA}$$



$\beta = 100$  for all BJT's

and  $|V_{BE}| = 0,6V$

First part  $\Rightarrow$

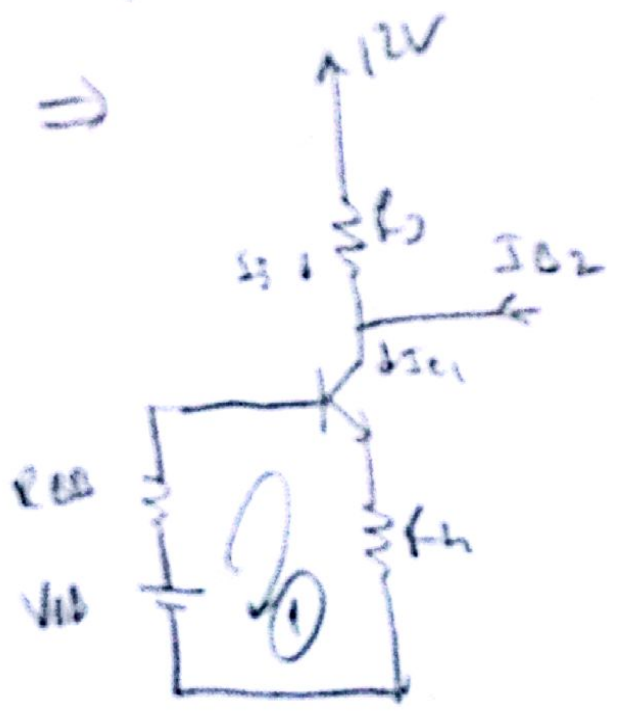


$$V_{BE} = V_{CC} \cdot \frac{R_2}{R_1 + R_2} = 3V$$

$$R_{B0} = R_1 || R_2 = 72k\Omega$$

Then we can assume  $I_{C1} = I_3$

$$\text{and } V_{CC} - \frac{I_C R_{C0}}{\beta} - V_{BE} - \frac{I_C}{\beta} (\beta + 1) \cdot R_E = 0$$

$$\Rightarrow I_{C1} = 0,131 \mu A$$

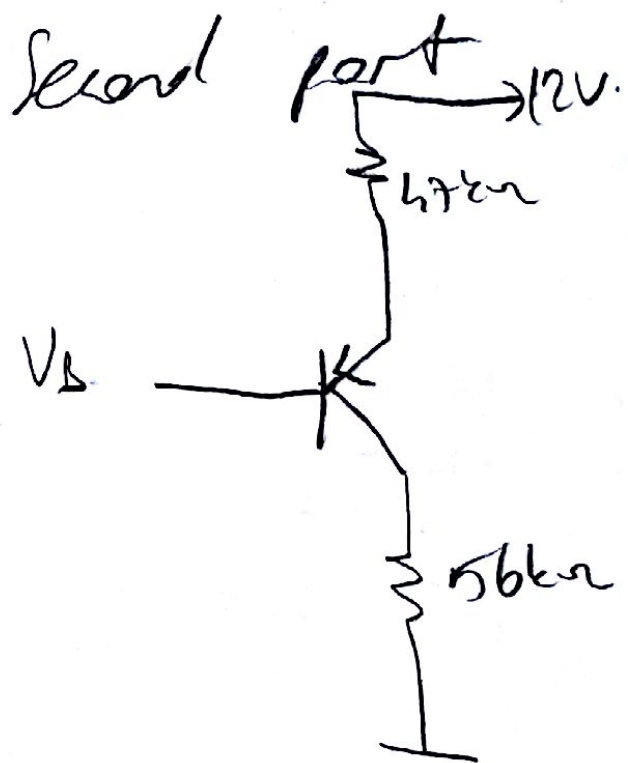

Write equation in the direction of loop 2

$$R_3 (I_{C2} - I_{B2}) = R_5 \cdot I_{E2} + V_{BE2}$$

$$\begin{array}{ccc} \downarrow & & \downarrow \\ \frac{I_{C2}}{\beta_F} & & \frac{I_{C2} (\beta_F + 1)}{\beta_F} \end{array}$$

$$\Rightarrow I_{C2} = 0,675 \text{ mA}$$

Write equation in the direction of loop-3

$$R_6 (I_{E2} - I_{B3}) = V_{BE3} + R_7 I_{E3}$$

$$\begin{array}{ccc} \downarrow & & \downarrow \\ \frac{I_{C2} (\beta_F + 1)}{\beta_F} & & \frac{I_{C3}}{\beta_F} \end{array} \quad \frac{\beta_F + 1}{\beta_F} \cdot I_{C3} \Rightarrow I_{C3} = 1,44 \text{ mA}$$

For simplicity, you can take all emitter currents are equal to collector currents!!!