

**Student Name:**

**Instructor: Mustafa Altun**

**Student ID:**

**Date: 11/1/2017**

# BLG231E Digital Circuits

## FINAL

*Duration: 120 Minutes*

*Grading: 1) 20%, 2) 15%, 3) 25%, 4) 40%*

*Exam is in closed-notes and closed-books format; calculators are allowed*

*For your answers please use the space provided in the exam sheet*

*GOOD LUCK!*



- 1) Consider a 6-variable Boolean function  $f = f_1(x_1, x_2, x_3, x_4) \cdot f_2(x_4, x_5, x_6)$  where  $f_1 = \prod (1,2,3,5,7,12,14)$  and  $f_2 = \prod (3,4,5,6,7)$ . Obtain a minimal product-of-sums (POS) expression for  $f$ .

- 2) Implement a 4-variable Boolean function  $f(x_1, x_2, x_3, x_4) = \sum (2,4,5,7,8,9,11,13,15)$  using a **single 4-to-1 multiplexer** and minimal number of **two-input NAND gates**. Use  $x_1$  and  $x_2$  as select input lines in the multiplexer. Use only variables  $x_1, x_2, x_3, x_4$  as inputs (**not their negated forms**).

3) Consider a flip-flop consisting of four NAND gates, shown below. Suppose that each of the NAND gates has a delay of **2ns**. Suppose that initial values of Q and Q' are 0 and 1, respectively.

a) Obtain a **minimal sum-of-products (SOP) expression for Q** in terms of previous Q, and inputs A and CLK.

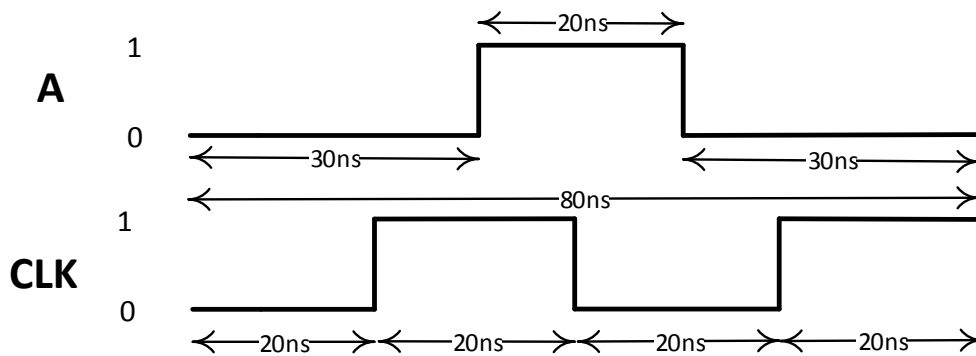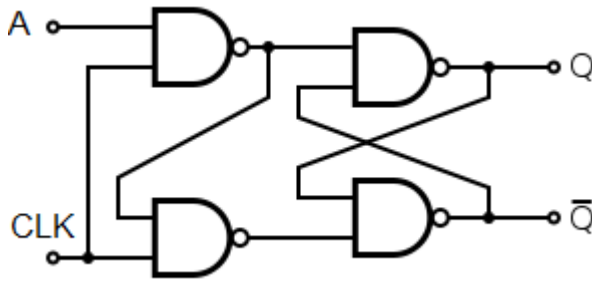b) Sketch the **waveforms at the outputs Q and Q'** if the input signals A and CLK shown below are applied.



- 4) Consider a **Mealy** machine based sequential circuit having one input **X** and one output **Z**. The output Z will be 0 except the input sequence **1101** are the last 4 inputs received on X. The circuit has 7 states defined as follows:

Input Sequence	State
.....00	A
.....11	B
.....001	C
.....010	D
.....110	E
.....0101	F
.....1101	G

- Obtain the state table and perform **state reduction**. After state reduction how many states remain?
- Draw the **state diagram** having the reduced states.
- Start designing the circuit with assigning 0's and 1's to the reduced states. Your design will be based on D-flip-flops. Derive minimal sum-of-products (SOP) Boolean expressions for the next states and the output in terms of the input and the current states.
- Draw the circuit using minimal number of **D-flip-flops**, and **AND**, **OR**, and **NOT** gates.

EXTRA PAGE FOR SOLUTIONS