

**Student Name:**

**Instructor: Mustafa Altun**

**Student ID:**

**Date: 09/12/2016**

# BLG231E Digital Circuits

## MIDTERM II

*Duration: 120 Minutes*

*Grading: 1) 20%, 2) 15%, 3) 35%, 4) 30%*

*Exam is in closed-notes and closed-books format; calculators are allowed*


*For your answers please use the space provided in the exam sheet*

**GOOD LUCK!**

- 1) Consider Boolean functions  $f_1(x_1, x_2, x_3) = \sum (0,1,3,5,6,7)$  and  $f_2(x_4, x_5, x_6) = \sum (2,3,4,5,6,7)$ . Implement  $f = f_1 + f_2$  using **two 3-to-8 decoders** and minimal number of **two-input NOR gates**.

- 2) Consider a comparator circuit that compares two binary inputs, A and B, and generates a binary output Y, such that  $Y=1$  if and only if these inputs are equal (i.e.  $A=B$ ).
- a) Implement a 1-bit comparator using **a single 4-to-1 multiplexer**.
- A and B are 1-bit numbers that results in 2 binary inputs and an output Y.
- b) Implement a 4-bit comparator using **four 4-to-1 multiplexers and a single AND gate**.
- A and B are 4-bit numbers  $A = A_3 A_2 A_1 A_0$  and  $B = B_3 B_2 B_1 B_0$  that results in 8 binary inputs and an output Y.

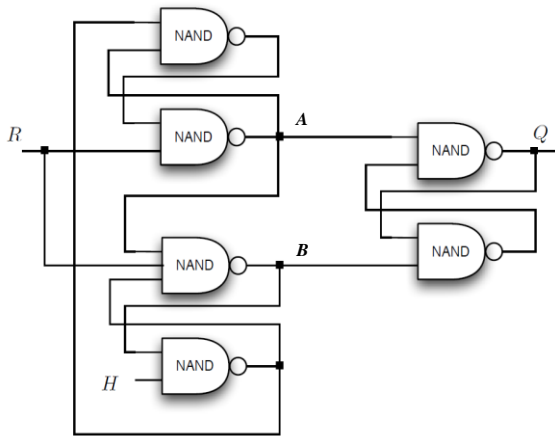3) Consider a sequential circuit shown below.



$R$	$H$	current $Q$	new $Q$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

- Fill out the above table by **inserting new  $Q$  values**. If **new  $Q$  values** cannot be precisely determined as logic 0 or logic 1, then express them using **current  $A$  and  $B$  values**.
- Find sum-of-products (SOP) expressions of **new  $Q$**  in terms of  **$R$ ,  $H$ , current  $Q$ , current  $A$ , and current  $B$** .

- 4) Consider a flip-flop consisting of one inverter, one XOR gate, and four NAND gates, shown below. Suppose that the inverter has a delay of **1ns**; each of the NAND gates has a delay of **3ns**; the XOR gate has a delay of **5ns**. Sketch the **waveforms at the outputs Q and Q'** if the input signals A and CLK shown below are applied. Suppose that initial values of Q and Q' are 0 and 1, respectively.

